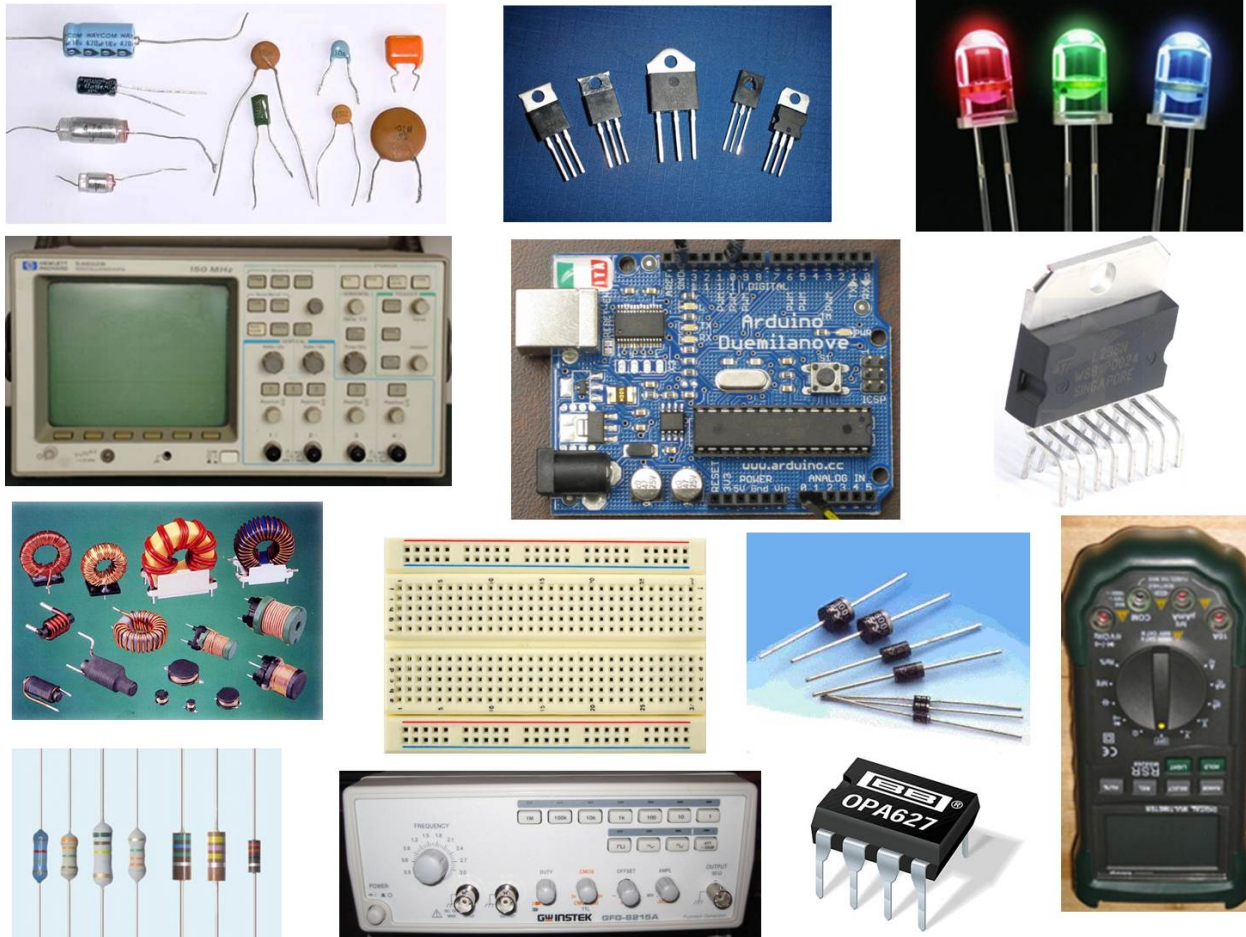



Op-Amp Example Problems with Solutions




For the following electrical system problems, the non-ideal op-amp model to be used is given below, where A is a very large number ($\approx 10^7$) and τ is the time constant.

$$V_{out} = \frac{A}{\tau s + 1} [V^+ - V^-] \quad i^+ = i^- = 0$$

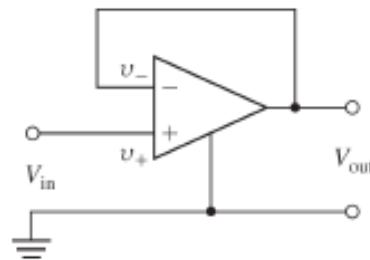
1. Show that the op-amp connection shown results in $V_{out} = V_{in}$ if the op-amp is ideal. Give the transfer function if the op-amp has the non-ideal model.



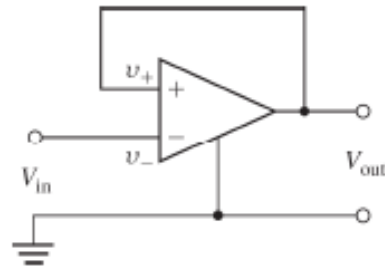
2. Show that, with the non-ideal op-amp model, the op-amp connection shown is unstable.





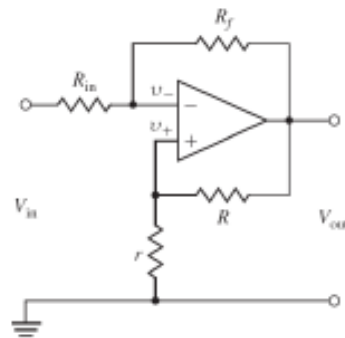
3. An op-amp connection with feedback to both the negative and positive terminals is shown. If the op-amp has the non-ideal transfer function, give the maximum value possible for the positive feedback ratio, $P = r/(r+R)$, in terms of the negative feedback ratio, $N = R_{in}/(R_{in}+R_f)$, for the circuit to remain stable.



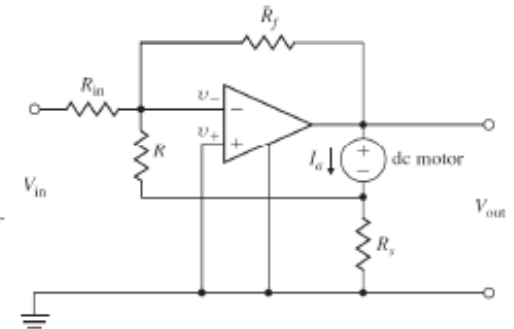
4. A common connection for a motor power amplifier is shown. The idea is to have the motor current follow the input voltage, and the connection is called a current amplifier. Model the motor as an inductor L_M and resistor R_M in series. Assume that the sense resistor R_S is very small compared with the feedback resistor R . For the ideal op-amp model, find the transfer function from V_{in} to I_a . Also show the transfer function when $R_f = \infty$.



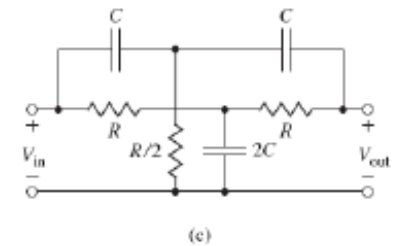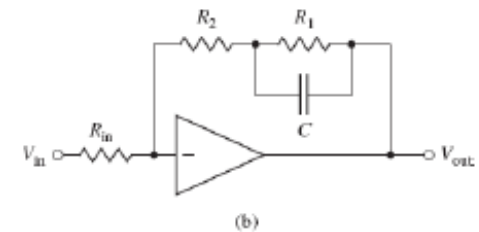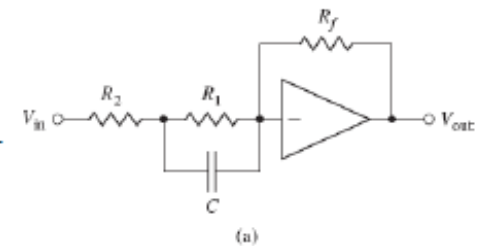5. Write the dynamic equations and find the transfer functions for the circuits shown: (a) lead circuit, (b) lag circuit, and (c) notch circuit. Use the ideal op-amp model.




1.

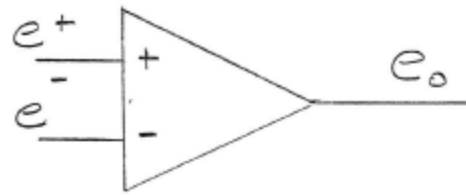

$$e_o = \frac{A}{\tau s + 1} (e^+ - e^-)$$

$$v^+ = v^- = 0$$

Realistic Op-Amp Model

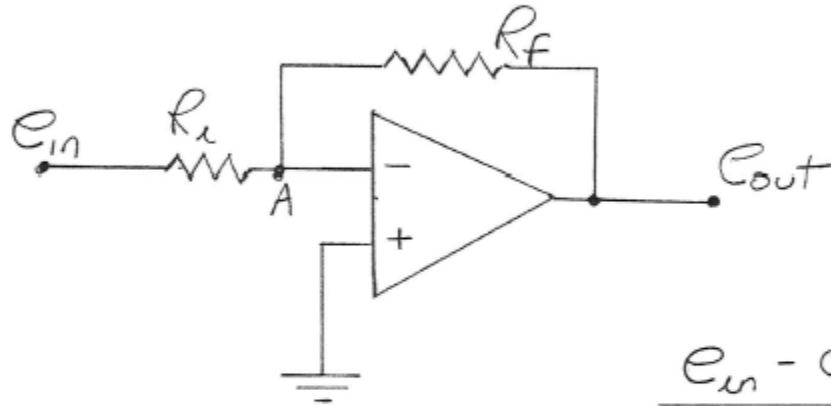

Inverting Op-Amp

Ideal Assumptions

$$e^+ = e^- \quad v^+ = v^- = 0$$

$$\frac{e_{in} - 0}{R_x} + \frac{e_{out} - 0}{R_f} = 0 \quad \text{KCL Node A}$$

$$\frac{e_o}{e_x} = - \frac{R_f}{R_x}$$

Non-Ideal

$$\frac{e_x - e^-}{R_x} + \frac{e_o - e^-}{R_f} = 0$$

$$e^- = \frac{e_x R_f + e_o R_x}{R_x + R_f} \Rightarrow e_o = \frac{A}{\tau s + 1} (e^+ - e^-)$$

$$e_o = \frac{A}{\tau s + 1} \left(0 - \frac{e_i R_f + e_o R_x}{R_x + R_f} \right)$$


Solve for e_o :

$$\frac{e_o}{e_i} = \frac{-A \left(\frac{R_f}{R_x + R_f} \right)}{\tau s + 1 + A \left(\frac{R_x}{R_x + R_f} \right)}$$

For : $A \rightarrow \infty$
 $\tau \rightarrow 0$

$$\frac{e_o}{e_i} = - \frac{R_f}{R_x}$$

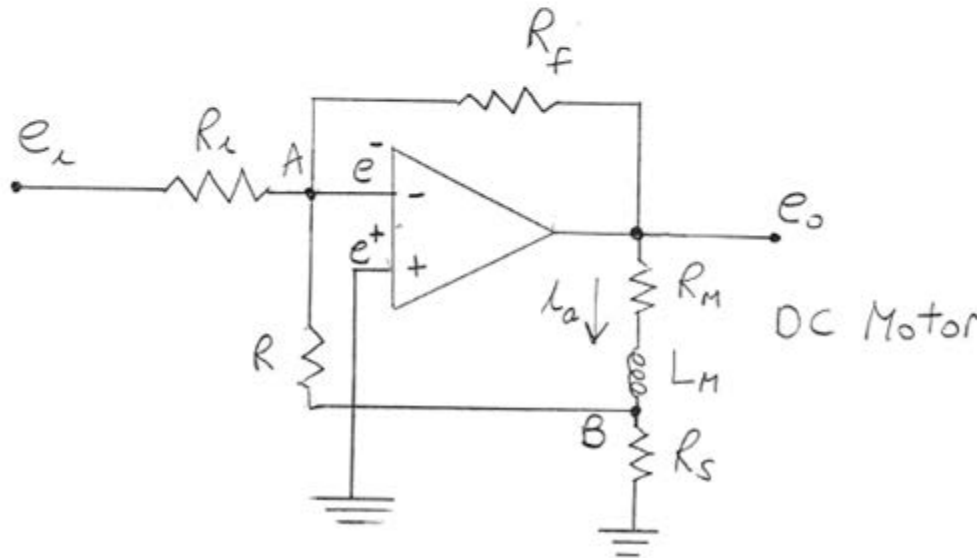2. Current Amplifier (Motor current follows input voltage)



Assume:

$$R_s \ll R$$

Ideal Op-Amp

$$e^+ = e^-$$

$$i^+ = i^- = 0$$

$$\text{KCL Node A: } \frac{e_i - 0}{R_i} + \frac{e_o - 0}{R_f} + \frac{e_B - 0}{R} = 0$$

$$e_A = e^- = e^+ = 0$$

$$\frac{e_i}{R_i} + \frac{e_o}{R_f} + \frac{e_B}{R} = 0$$

$$\text{KCL Node B: } i_a + \frac{0 - e_B}{R} + \frac{0 - e_B}{R_s} = 0$$

$$e_B = \frac{R R_s}{R + R_s} i_a = \frac{R_s}{1 + R_s/R} i_a \approx R_s i_a$$

for $R_s \ll R$

DC Motor Dynamics

$$J_m \ddot{\theta}_m + b \dot{\theta}_m = K_t i_a$$

$$J_m \dot{\omega}_m + b \omega_m = K_t i_a$$

$$(J_m s + b) \omega_m = K_t i_a$$

} Mechanical

$$\omega_m = \frac{K_t i_a}{J_m s + b}$$

$$(\omega_m = \dot{\theta}_m)$$

$$e_a - i_a R_a - L_a \dot{i}_a - K_e \omega_m = 0$$

$$e_a = i_a L_a + L_a \dot{i}_a + K_e \omega_m$$

$$(L_a s + R_a) i_a + K_e \omega_m = e_a$$

} Electrical

$$e_o - e_f = e_a \text{ (motor armature voltage)}$$

$$e_o - R_s i_a = e_a$$

$$e_o = i_a R_s + (L_a s + R_a) i_a + K_e \omega_m$$

$$e_o = i_a R_s + (L_a s + R_a) i_a + K_e \left(\frac{K_t i_a}{J_m s + b} \right)$$

Let's go back to KCL for Node A:

$$\frac{e_i}{R_i} + \frac{e_o}{R_f} + \frac{e_b}{R} = 0$$

$$\frac{e_i}{R_i} + \frac{i_a}{R_f} \left[L_a s + R_a + R_s + \frac{K_e K_t}{J_m s + b} \right] + \frac{R_s i_a}{R} = 0$$

In steady state $s \rightarrow 0$


$$\frac{e_i}{R_i} + \frac{i_a}{R_f} \left[R_a + R_s + \frac{K_e K_t}{b} \right] + \frac{R_s i_a}{R} = 0$$

$$\frac{e_x}{R_x} + \left[\frac{R_a}{R_f} + \frac{R_s}{R_f} + \frac{K_e K_t}{b R_f} + \frac{R_s}{R} \right] i_a = 0$$

If $R_f \rightarrow \infty$ Then $\frac{e_x}{R_x} + \frac{R_s i_a}{R} = 0$

$$\frac{i_a}{e_x} = - \frac{R}{R_x R_s}$$

3.

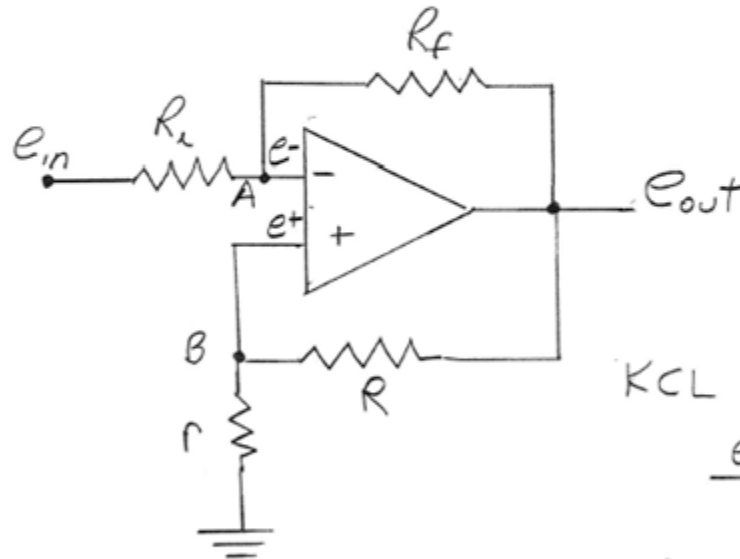

Non-Ideal TF

$$e_o = \frac{A}{1+s+1} (e^+ - e^-)$$

KCL Node A

$$\frac{e_x - e^-}{R_x} + \frac{e_o - e^-}{R_f} = 0$$

KCL Node B

$$\frac{e_o - e^+}{R} + \frac{0 - e^+}{r} = 0$$

Define:

$$P = \frac{r}{r+R}$$

$$N = \frac{R_x}{R_x + R_f}$$

$$\frac{e_x - e^-}{R_x} + \frac{e_0 - e^-}{R_f} = 0 \Rightarrow \frac{e_x}{R_x} + \frac{e_0}{R_f} = e^- \left(\frac{1}{R_x} + \frac{1}{R_f} \right)$$

$$e^- = \frac{R_f}{R_x + R_f} e_x + \frac{R_x}{R_x + R_f} e_0$$

$$e^- = (1-N)e_x + N e_0$$

$$\frac{e_0 - e^+}{R} + \frac{0 - e^+}{r} = 0 \Rightarrow \frac{e_0}{R} = e^+ \left(\frac{1}{R} + \frac{1}{r} \right)$$

$$\frac{e_0}{R} = e^+ \left(\frac{1}{R} + \frac{1}{r} \right)$$

$$e^+ = \frac{r}{R+r} e_0 = p e_0$$

$$e_0 = \frac{A}{\tau s + 1} (e^+ - e^-) \Rightarrow$$

$$e_0 = \frac{A}{\tau s + 1} (p e_0 - (1-N)e_x - N e_0)$$

$$e_0 = \frac{A}{\tau s + 1} ((p-N)e_0 - (1-N)e_x)$$

$$e_0 \left[1 - \frac{A}{\tau s + 1} (p-N) \right] = \frac{-A}{\tau s + 1} (1-N) e_x$$

$$\frac{e_0}{e_x} = \frac{A(N-1)}{\tau s + 1 - A(p-N)}$$

Stability

$$1 - A(p-N) > 0$$



$$1 > A(p-N)$$

$$A(N-p) > -1$$

$$N-p > -\frac{1}{A}$$

$$\underline{\underline{p < N + \frac{1}{A}}}$$

4.

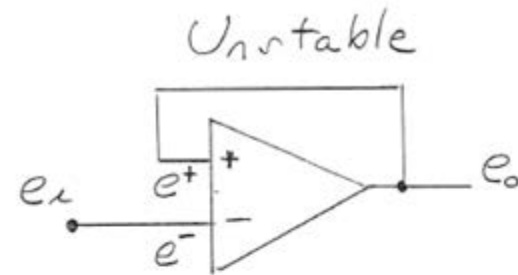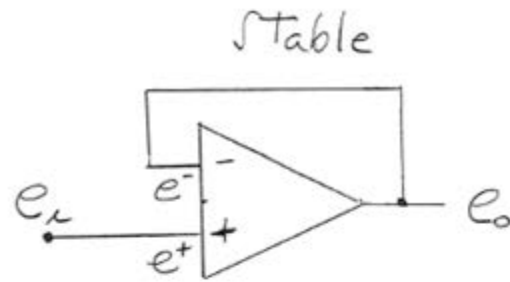

$$e_o = \frac{A}{\tau s + 1} (e^+ - e^-)$$

$$e_o = \frac{A}{\tau s + 1} (e_x - e_o)$$

$$e_o \left(1 + \frac{A}{\tau s + 1} \right) = \frac{A}{\tau s + 1} e_x$$

$$\frac{e_o}{e_x} = \frac{A}{\tau s + 1 + A}$$

$$\tau s + 1 + A = 0$$

$$s = \frac{-1 - A}{\tau}$$

Negative real root
stable

$$e_o = \frac{A}{\tau s + 1} (e_o - e_x)$$

$$e_o \left(\frac{A}{\tau s + 1} - 1 \right) = \frac{A}{\tau s + 1} e_x$$


$$\frac{e_o}{e_x} = \frac{A}{-\tau s - 1 + A}$$

$$-\tau s - 1 + A = 0$$

$$s = \frac{A - 1}{\tau}$$



positive real root
unstable

5.

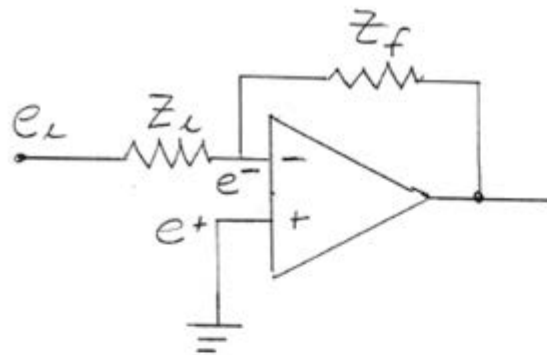

$e^+ = e^-$
 $i^+ = i^- = 0$ Ideal Op-Amp

$$\frac{e_o}{e_i} = - \frac{Z_f}{Z_x}$$

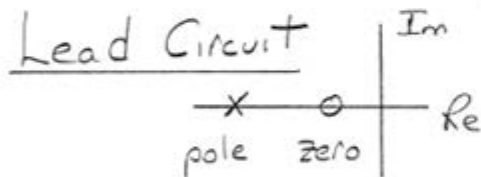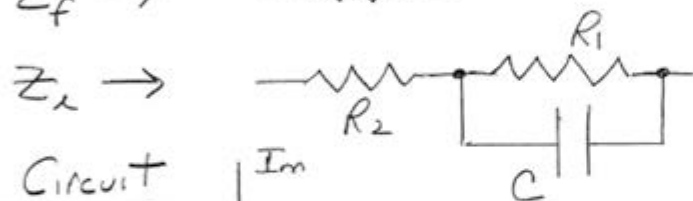


$$Z_f = R_f$$

$$Z_x = R_2 + \frac{R_1/Cs}{R_1 + 1/Cs}$$


$$\frac{e_o}{e_i} = \frac{-\frac{R_f}{R_2} (s + \frac{1}{R_1 C})}{(s + \frac{1}{R_1 C} + \frac{1}{R_2 C})}$$

zero: $s = -\frac{1}{R_1 C}$

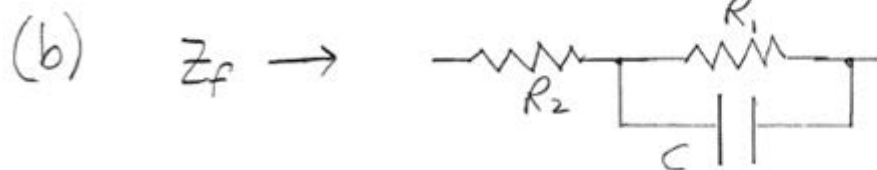pole: $s = -\frac{1}{R_1 C} - \frac{1}{R_2 C}$



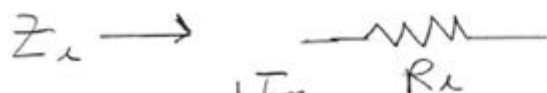
$$Z_f = R_2 + \frac{R_1/Cs}{R_1 + 1/Cs}$$




$$Z_x = R_x$$
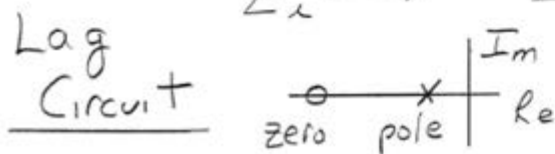
$$\frac{e_o}{e_i} = \frac{-\frac{R_2}{R_x} (s + \frac{1}{R_1 C} + \frac{1}{R_2 C})}{(s + \frac{1}{R_1 C})}$$



pole and zero are reversed.

(c)

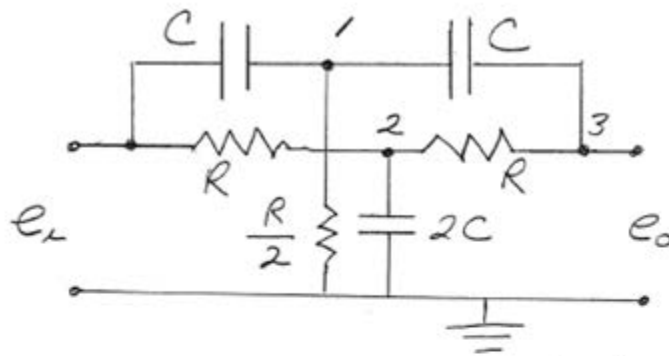

Notch Circuit

KCL

$$\text{Node 1: } C \frac{d}{dt} (e_i - e_1) + \frac{0 - e_1}{R/2} + C \frac{d}{dt} (e_o - e_1) = 0$$

$$\text{Node 2: } \frac{e_i - e_2}{R} + 2C \frac{d}{dt} (0 - e_2) + \frac{e_o - e_2}{R} = 0$$

$$\text{Node 3: } C \frac{d}{dt} (e_1 - e_o) + \frac{e_2 - e_o}{R} = 0$$

Laplace Transformed Equations

$$\begin{cases} Cs(e_i - e_1) - \frac{2e_1}{R} + Cs(e_o - e_1) = 0 \\ \frac{e_i - e_2}{R} - 2Cs e_2 + \frac{e_o - e_2}{R} = 0 \\ Cs(e_1 - e_o) + \frac{e_2 - e_o}{R} = 0 \end{cases}$$

Matrix Representation of Equations

$$\begin{bmatrix} -2Cs - \frac{2}{R} & 0 & Cs \\ 0 & -2Cs - \frac{2}{R} & \frac{1}{R} \\ Cs & \frac{1}{R} & -Cs - \frac{1}{R} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_0 \end{bmatrix} = \begin{bmatrix} -Cs \\ -\frac{1}{R} \\ 0 \end{bmatrix} e_x$$

Solve for e_0

$$\frac{e_0}{e_x} = \frac{s^2 + \frac{1}{R^2C^2}}{s^2 + \frac{4}{RC}s + \frac{1}{R^2C^2}}$$